

## Lab-8 (11<sup>th</sup> and 12<sup>th</sup> September)

### ECE270 - Embedded Logic Design



#### Tasks to be performed in this lab with homework

**Board:** Basys 3 Board, Xilinx Artix – 7 FPGA (XC7A35T-1CPG236C)

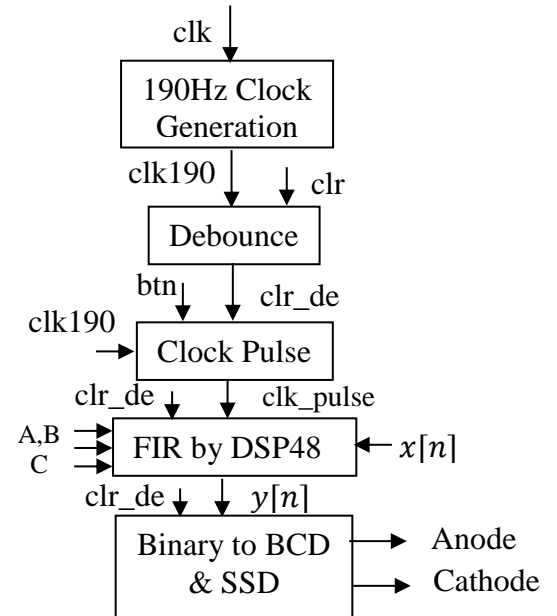 1. Design and implement a 3-tap FIR filter with following specifications:



- The value of  $x[n]$  is to be taken from switches, sw[2:0].
- To perform addition operation, the weights  $b_0$ ,  $b_1$  and  $b_2$  are taken as 1.  
Therefore,  $y[n] = x[n] + x[n - 1] + x[n - 2]$
- The flip flops should work on a clock pulse.

Convert the output,  $y[n]$  to the BCD format and display it on 7-segment display.



 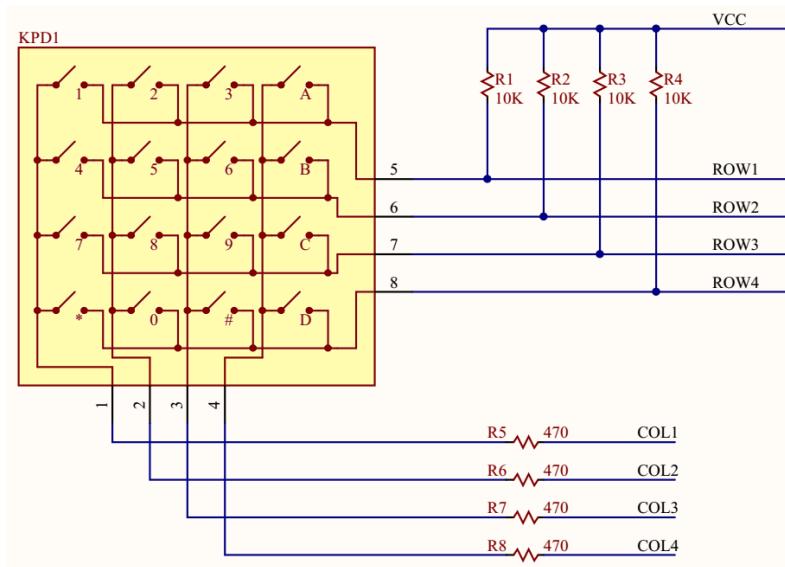2. Write a Verilog code which connects Keypad to Basys3 board via PMOD and displays the key press on the 7 segment display.





- Write a Verilog code which connects a keypad and external 7 segment display to the Basys 3 board via PMOD ports. Instead of using switches in Ques. 1, use the key press on the keypad to enter the value of  $x[n]$  that ranges from 0 to 9. Display the output  $y[n]$  to an external 7-segement display.

Hint: <https://reference.digilentinc.com/reference/pmod/pmodssd/reference-manual>