

Lab-6 (25th and 27th September)
ECE270 - Embedded Logic Design

Board: Basys 3 Board, Xilinx Artix – 7 FPGA (XC7A35T-1CPG236C)

Tasks:

1. Design and code an FSM to detect an overlapping sequence of '11011' as
 - a) Moore machine.
 - b) Mealy machine.Compare the resource requirement for both machines.
2. Design and code an FSM to detect a non-overlapping sequence of '10101' as
 - a) Moore machine.
 - b) Mealy machine.Compare the resource requirement for both designs.

Design details:

- The input sequence will be given with the help of two push buttons.
- One of the push button will correspond to an input of '1' and other to an input of '0'.
- Use debouncing circuit to generate a clean pulse if any of the push button is pressed.
- Use this pulse to sample the inputs of the sequence detector FSM module.
- Whenever the desired sequence is detected, one of the LEDs on board should light up.
- The output LED should remain low whenever the input sequence is invalid.

Specific submission requirements:

- In the document to be submitted on Backpack, attach the FSM for both Mealy and Moore machines in the document along with your codes.