
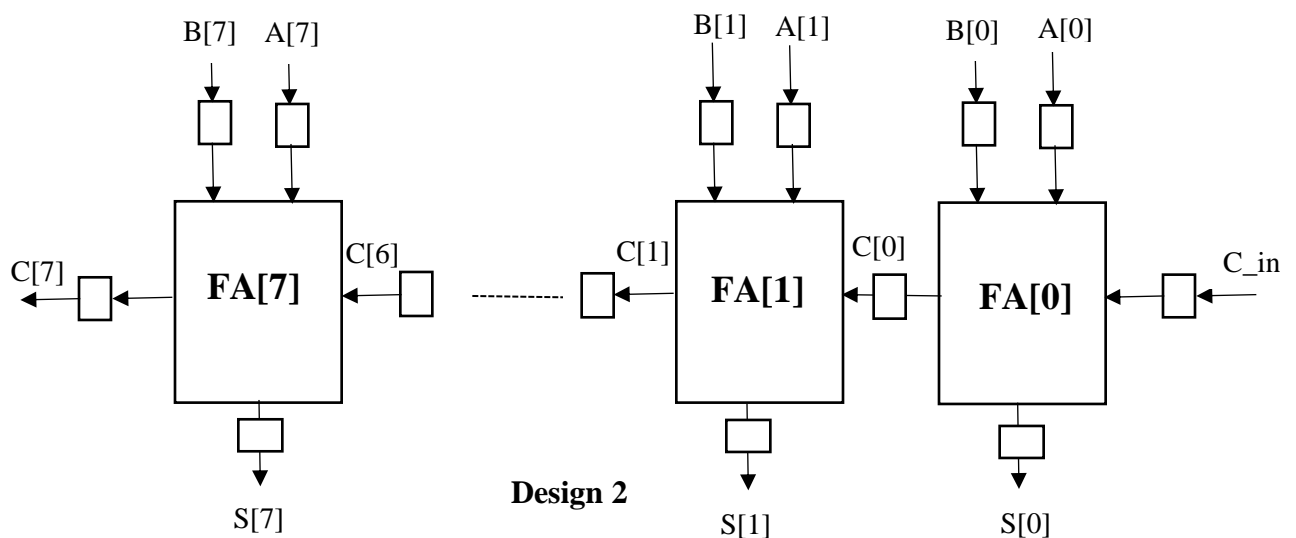


# ECE270 - Embedded Logic Design

**Board:** Basys 3 Board, Xilinx Artix – 7 FPGA (XC7A35T-1CPG236C)

 
1. Design and implement an 8-bit full adder. Pass both 8-bit inputs and outputs through flip flops.





- Determine the maximum clock frequency of design 2 that meets the timing constraints. Compare it with design 1.

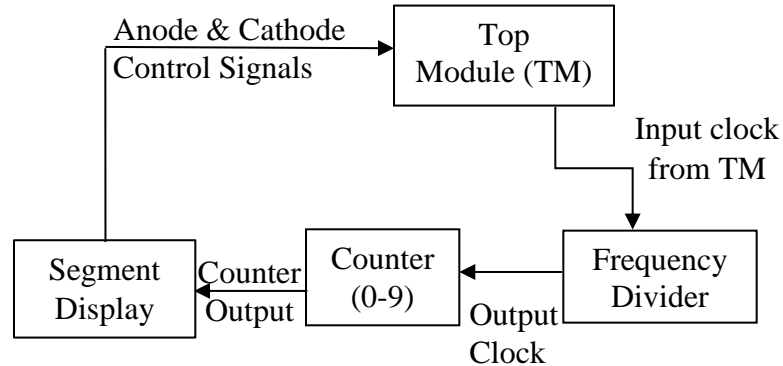
## PART 2: Seven Segment Display

- Design a counter that counts from 0 to 9. Display the count on seven segment display of Basys 3 board. Note that frequency divider will divide the input clock by  $2^{25}$ .




## 7-Segment Display

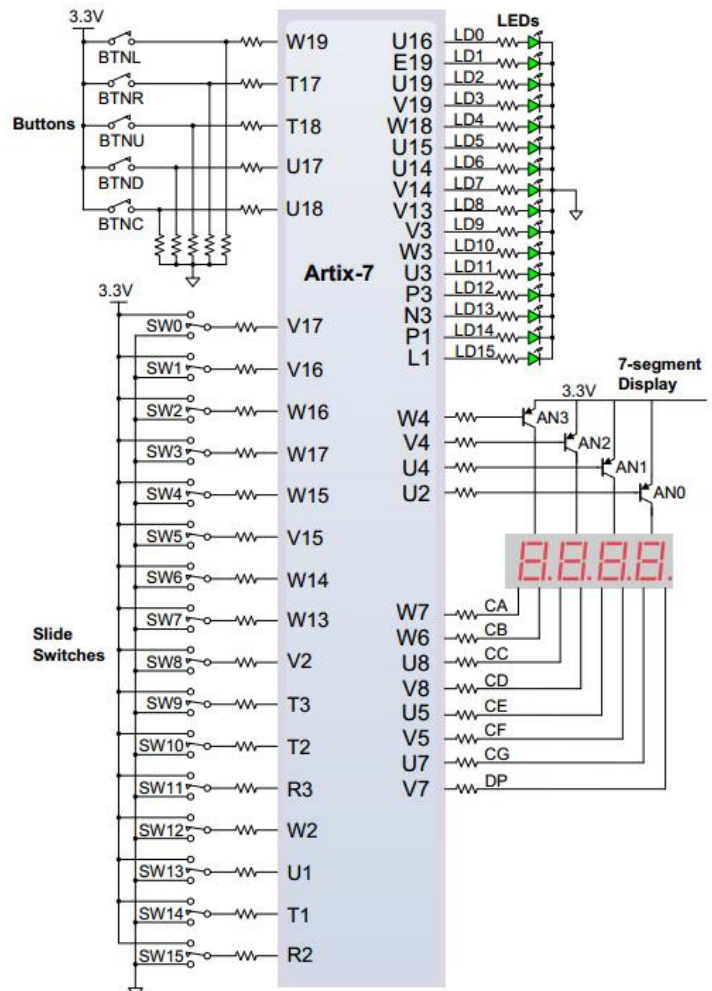 

 


 6. Design and implement an 8-bit binary to BCD converter. Note that frequency divider will divide the input clock by  $2^{25}$ .



Reference: <http://www.tkt.cs.tut.fi/kurssit/1426/S12/Ex/ex4/Binary2BCD.pdf>

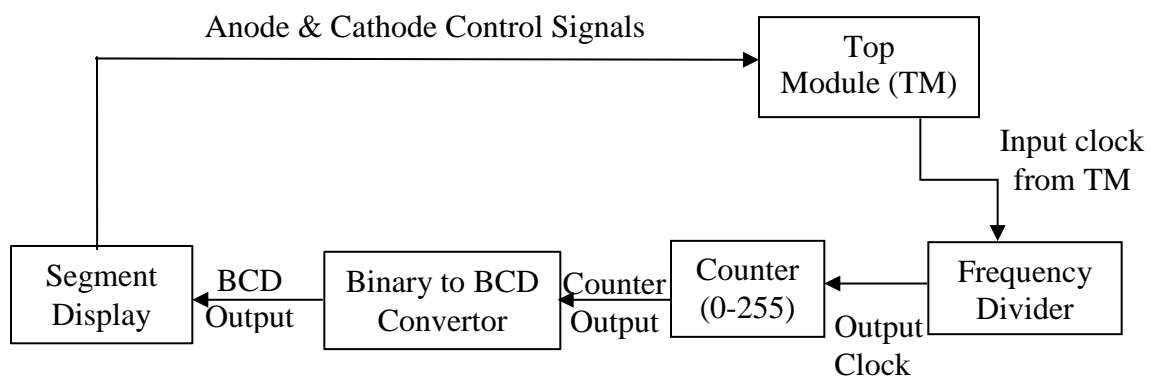7. Design a counter that counts from 00000000 to 11111111. Convert this 8-bit binary number to a BCD number. Display the count from 0 to 255 on the seven segment display. Note that the frequency divider will generate a clock of 1Hz. (Hint: Use time multiplexing to display different digits at different decimal position.)



Reference: [https://reference.digilentinc.com/\\_media/basys3:basys3\\_rm.pdf](https://reference.digilentinc.com/_media/basys3:basys3_rm.pdf)